
 


ECEN 350 – Equation Sheet 2 (12/27/2024)

 BJT Cutoff Region: The Base-Emitter junction is not forward biased, resulting in the transistor behaving like an open switch between the Collector and Emitter.



BJT Active Region: The Base-Emitter junction is forward biased, with the Collector-Base Junction not forward biased, resulting in the transistor approximating a dependent current source with $I_C = \beta I_B$. The active region is the desired operating region for transistor amplifiers.




BJT Saturation Region: BJT saturation occurs when the Base-Emitter junction is forward biased, with the Collector-Base junction also slightly forward biased. BJT saturation, implies that $V_{CE} \leq 0.3$ V for an npn BJT and $V_{EC} \leq 0.3$ V for a pnp BJT. The 1st approximation for BJT saturation is a closed switch between Collector and Emitter.



For a BJT in the active region:

$$\alpha \triangleq I_C/I_E, \beta \triangleq I_C/I_B$$

 
$$I_C = \beta I_B, I_E = I_C + I_B \approx I_C$$



Good coupling: $X_c < 0.1R$, where R is the equivalent input or output resistance, with $X_c = 1/2\pi fC$.


Good bypassing: $X_c < 0.1R$, where R is the equivalent resistance of the parallel element to short out for ac signals.

 Small – Signal Analysis: $i_c = \beta i_b, i_e = \beta i_b, r'_e = \frac{25 \text{ mV}}{I_E}$.



V_{BE} Current Limit: $I_{limit} = \frac{0.66 \text{ V}}{R_{cl}}$.

 Darlington Configuration: $I_{B2} \approx I_{E2}/\beta_2, I_{B1} \approx I_{E1}/\beta_1, \beta_{total} = \beta_1\beta_2$.




Voltage Divider Bias Amplifier with ac and dc Emitter Resistors

$$A_v = \frac{-r_c}{r'_e} \text{ for } r_e = 0.$$

$$A_v = \frac{-r_c}{r'_e + r_e} \text{ for } r_e \neq 0.$$

$$Z_{in} = R1 \parallel R2 \parallel Z_{in(base)}.$$


$$Z_{in(base)} = \beta(r'_e + r_e).$$

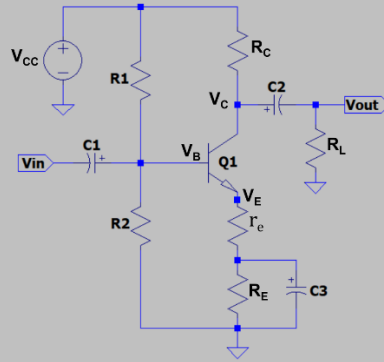


Common Collector (Emitter Follower) Amplifier

$$A_v = \frac{r_e}{r'_e + r_e} \leq 1.$$

$$Z_{in(base)} = \beta(r'_e + r_e).$$

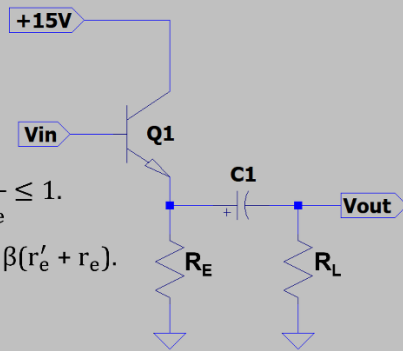

Differential to SE Amplifier

 

$$A_v = \frac{R_C}{2r'_e}.$$

$$CMRR = \frac{A_v}{A_{v,CM}}.$$

$$CMRR_{dB} = 20 \log(CMRR)$$

n-channel Enhancement Mode MOSFET

$$V_{GS} < V_T, I_D = 0. \text{ (Cutoff),}$$

$$\text{For } V_{GS} \geq V_T, 0 < V_{DS} < V_{GS} - V_T. \text{ (Ohmic)}$$

$$I_D = \beta_n \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right], \text{ where } \beta_n = \mu_n C_{ox} \frac{W}{L}.$$

$$\text{For } V_{GS} \geq V_T, V_{DS} \geq V_{GS} - V_T. \text{ (Transistor Saturation)}$$

$$I_D = \frac{\beta_n}{2} (V_{GS} - V_T)^2.$$

p-channel Enhancement Mode MOSFET


$$V_{SG} < |V_T|, I_D = 0. \text{ (Cutoff),}$$

$$\text{For } V_{SG} \geq |V_T|, 0 < V_{SD} < V_{SG} - |V_T|. \text{ (Ohmic)}$$

$$I_D = -\beta_p \left[(V_{SG} - |V_T|)V_{SD} - \frac{V_{SD}^2}{2} \right], \text{ where } \beta_p = \mu_p C_{ox} \frac{W}{L}.$$

$$\text{For } V_{SG} \geq |V_T|, V_{SD} \geq V_{SG} - |V_T|. \text{ (Transistor Saturation)}$$

$$I_D = -\frac{\beta_p}{2} (V_{SG} - |V_T|)^2.$$

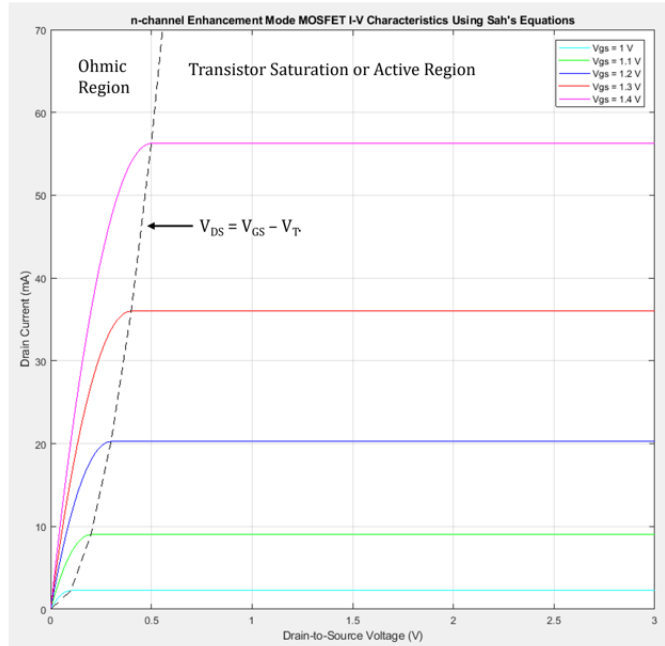

CMOS Dynamic Power Dissipation: $P_{\text{Dynamic}} = C_{\text{Load}} N_{\text{sw}} V_{\text{DD}}^2 f$, where V_{DD} is the supply Voltage, N_{sw} is the number of nodes switching and f is the switching frequency.

Sizing CMOS Digital Logic: $W_p = \frac{\mu_n}{\mu_p} W_n$, where μ is mobility, W_n is the relative width of the n-channel transistor and W_p is the relative width of the p-channel transistor.