

Brodric Young
ECEN 350
Diode Rectifier Lab

ECEN 350 – Diode Rectifier Lab (60 points)
(jas, Diode Rectifier Lab.docx, 12/28/2024)

There are both simulation and hardware portions to this lab, and you can work in pairs if desired on the hardware portion, with no three person teams allowed. Each class member is to submit an electronic version of a lab report for credit for this lab. The goal of your lab report is to provide sufficient documentation so that the lab can be repeated if necessary. For your lab report, add a cover page, your results, along with your answers to the **Discussion and Conclusions** questions to this instruction document. Your cover page is to include class, lab title, author and lab partner. If you worked in a pair, you can share all measured data with your lab partner. However, any simulations along with your **Discussion and Conclusions** section is to be uniquely yours and not a copy of your lab partners. A grading rubric for this lab is included at the end of this document. The rubric does not need to be included in your lab report.

Purpose: To better understand transformers along with commonly used diode rectification circuitry utilizing silicon pn junction diodes.

Parts and Equipment:

- 2 – 1N4007 Diodes
- 1 - 4.7 k Ω Resistor
- 1 - 10 μ F 50 V capacitor (Aluminum Electrolytic).
- 1 - 120 V rms to 28 V rms Step-Down Transformer.
- 1 - VirtualBench Measurement System and Computer
- 1 - Breadboard.

VirtualBench Oscilloscope:

The VirtualBench Oscilloscope User Interface Screen with Channel 1 (red) connected to a 1 kHz sine wave with 5 V peak-to-peak output amplitude is illustrated in **Figure 1** below. Several automatic waveform measurements are available for the oscilloscope, controlled by means of the Waveform Measurement Icon illustrated below in **Figure 1**. Two waveform cursors are also available, controlled by the Waveform Cursor Icon, illustrated below in **Figure 1**.

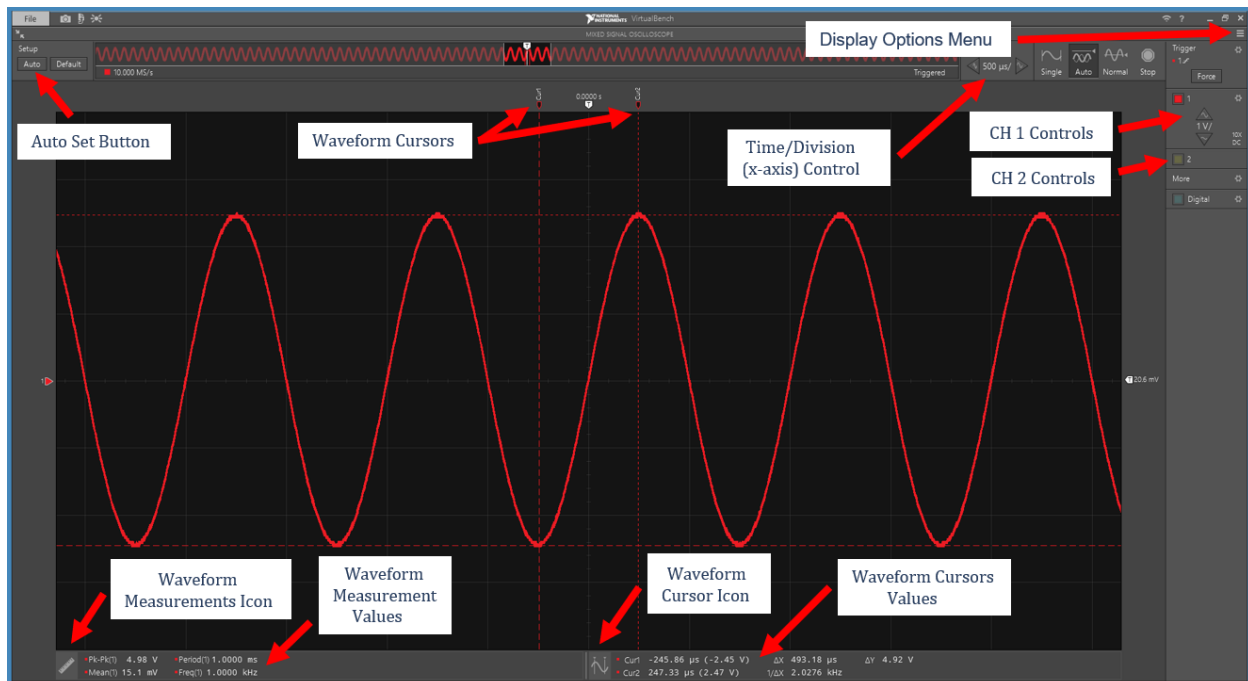


Figure 1: VirtualBench Oscilloscope User Interface Pane Example.

The **Auto** button illustrated in the upper left-hand corner of the screen in **Figure 5**, provides for automatic waveform adjustment. The **Auto** setup button is useful whenever you lose track of the waveform being measured or connect the probes to a new waveform.

In its simplest form a waveform trigger is a voltage level that provides a reference point for the waveform display. The VirtualBench oscilloscope acquires a sizeable portion of waveform voltage versus time data, then displays the results utilizing a waveform reference point determined by the waveform trigger. This acquisition and display process is repeated over and over, resulting in periodic waveforms appearing stationary when properly triggered. So oscilloscope waveform triggering provides for periodic (repeating) waveforms to look stationary, which is useful for waveform viewing and analysis. Periodic signals with non-negligible random voltage variations (noise) often appear to jitter back and forth on an oscilloscope screen, because the noise causes the trigger reference point to occur at slightly different portions of the waveform each time the waveform is displayed. A Noise Reject triggering Hysteresis option, available in the **Trigger Settings** pane, helps minimize waveform jitter on noisy signals by noise filtering.

Oscilloscopes provide voltage triggering on either rising (increasing) or falling (decreasing) waveform voltages, referred to as Rising or Falling edge triggering. The **Auto** setup button of the VirtualBench oscilloscope sets the trigger conditions for a given waveform, which is sufficient for most measurements, although sometimes specialized triggering conditions are desired, requiring the user to manually adjust the triggering using the Trigger menu.

The VirtualBench oscilloscope offers **Auto**, **Normal** and **Single** triggering modes, along with a **Stop** mode that stops waveform triggering to freeze the current waveform on the screen. In the **Normal** trigger mode, the oscilloscope refreshes a displayed waveform after a valid trigger occurs. If a valid trigger never occurs, usually because the trigger level is incorrectly adjusted for a given waveform, then the waveform never refreshes, making it difficult to find the waveform being measured to correctly adjust the trigger. **Auto** trigger comes to the rescue in these circumstances. In **Auto** trigger mode, the oscilloscope waits only so long for a valid waveform trigger, then automatically triggers and displays the captured waveform if the predetermined wait time expires before receiving a valid trigger. This helps in hunting for waveforms by providing some user feedback regarding the waveform to be measured. The **Auto** trigger mode is the default triggering mode for the VirtualBench oscilloscopes. The **Auto** button illustrated in the upper left-hand corner of the screen in **Figure 1**, sets the oscilloscope triggering to **Auto** and also provides for automatic adjustment of the amplitude and time scales in order to better view the waveform.

Single triggering is useful for capturing and then freezing on the screen a one-time event. If you try to view a one-time event using **Auto** triggering, the oscilloscope will display the event upon receiving a valid trigger, but then refresh the display with a new waveform upon the next trigger. So, each of the three VirtualBench triggering modes have their place in waveform measurements, as does the **Stop** triggering mode when one does not want the currently displayed waveform to be replaced by a new waveform capture.

Step-Down Transformer:

The standard US AC power is 120 V rms at 60 Hz, which translates to $(120\text{ V})\sqrt{2} = 170\text{ V}$ peak. This AC voltage is typically stepped down to safer voltages by means of a step-down transformer prior to rectification. A step-down transformer as shown in **Figure 2**, is to be used for this lab. This center-tapped transformer plugs into the 120 V ac rms in the wall and steps the voltage down to approximately 14 V ac rms ($\approx 21\text{ V}$ peak), between the black center tap terminal and either of the red output terminals. The corresponding voltage between the two red output terminals is then approximately 28 V ac rms ($\approx 42\text{ V}$ peak).

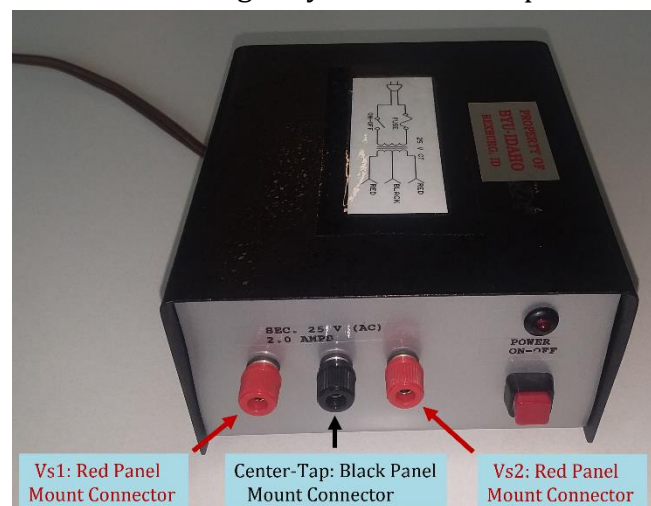


Figure 2: Center-Tapped Transformer to Use in the Diode Rectifier Lab.

A schematic of the center-tapped transformer is illustrated below in **Figure 3**.

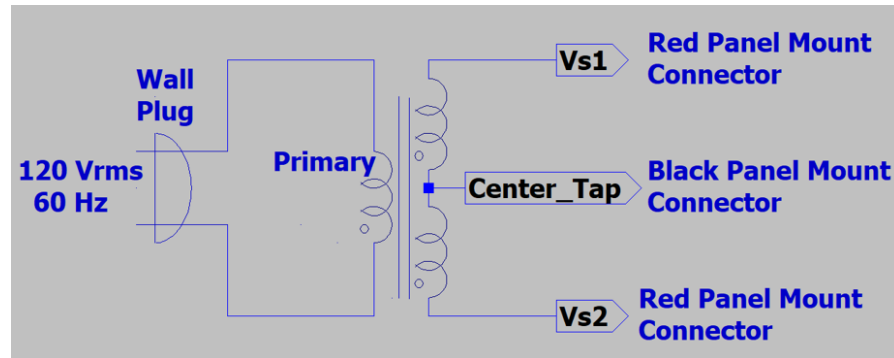



Figure 3: Center-Tapped Step-Down Transformer Schematic.

Procedure:

Part 1 – Center-Tapped Transformer

1. Connect the oscilloscope probe with the red marking bands to Channel 1 (CH 1) and the oscilloscope probe with the yellow marking bands to Channel 2 (CH 2) on the VirtualBench CH 1 and CH 2 oscilloscope BNC connectors. Make sure the slide switches at the probe tip end of the oscilloscope probes are set to 10X versus 1X.
2. Start up the VirtualBench interface software and for the CH 1 and CH2 settings  make sure that both are set for DC coupling and 10X probe attenuation.
3. Connect the CH 1 and CH 2 oscilloscope probes to the two red output connectors of the center tapped transformer, with both probe ground clips connected to the black center-tapped connector. It doesn't matter which probe is connected to which red connector.
Warning: The oscilloscope probe ground clips are connected to earth ground through the oscilloscope AC power cord, meaning that connecting the alligator ground clip to a circuit node shorts that node to earth ground.
4. Turn on the transformer and use the **Auto Set** button in the VirtualBench user interface to display the two waveforms, which should look like the screen capture illustrated in **Figure 4** below.
5. Enable the **Mean**, **RMS**, **Peak-to-peak** and **High** VirtualBench measurement functions for both CH 1 and CH 2 measurements, with the **High** measurement corresponds to the peak voltage value.
6. After the measured values are properly displayed, select **Stop**, to stop the acquisitions, and then record the measured **Mean**, **Peak-to-peak**, **RMS**, and **High** values for both V_{s1} and V_{s2} in **Table 1** below. (8 points.)

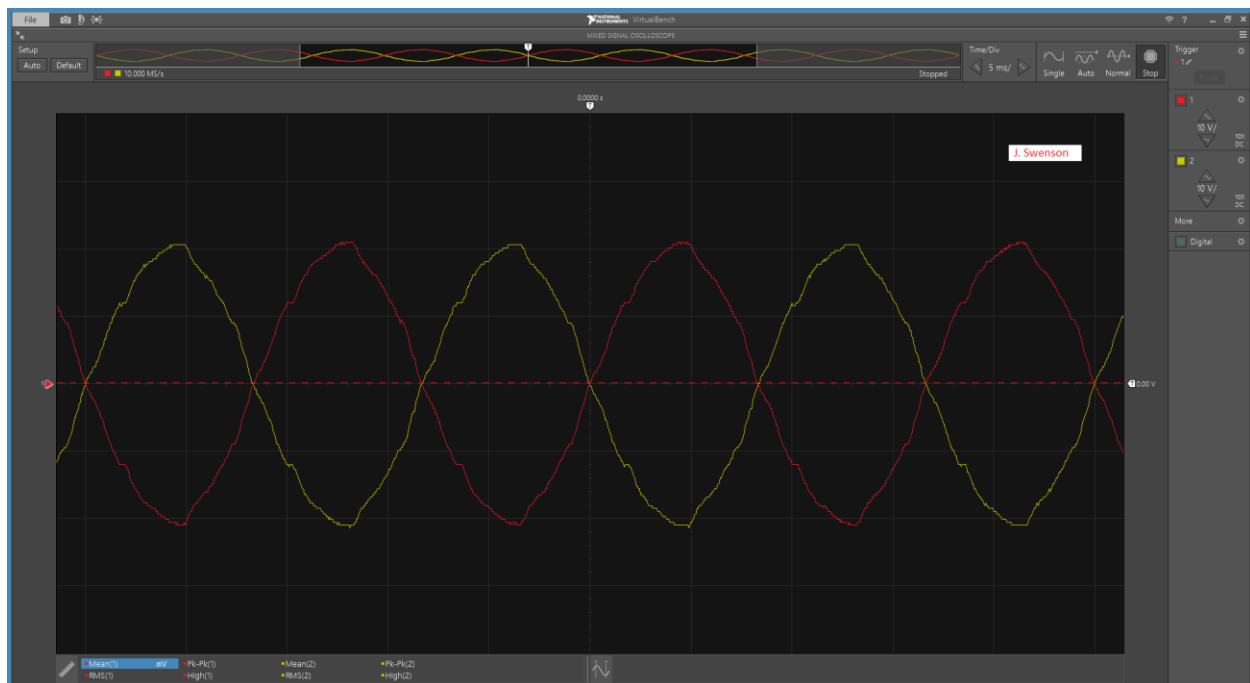


Figure 4: Output Waveforms from the Center-Tapped Step-Down Transformer Schematic.

Table 1: Measured Center-Tapped Transformer Values

V_{s1_mean}	V_{s1_rms}	V_{s1_pk-pk}	V_{s1_pk}	V_{s2_mean}	V_{s2_rms}	V_{s2_pk-pk}	V_{s2_pk}
48.8 mV	14.6 V	43.6 V	21.8 V	9.58 mV	14.5 V	43.6 V	21.8 V

Part 2 – Hardware Full-Wave Rectifier

1. With the transformer turned off, connect up a full-wave center tapped transformer rectifier as shown in **Figure 5** below. **Be careful to connect the polarized capacitor C1 with the proper polarity to prevent this capacitor from exploding!** On the physical capacitor the lead adjacent to a negative polarity stripe on the body of the part indicates the negative lead, which corresponds to the curved plate on the schematic symbol.

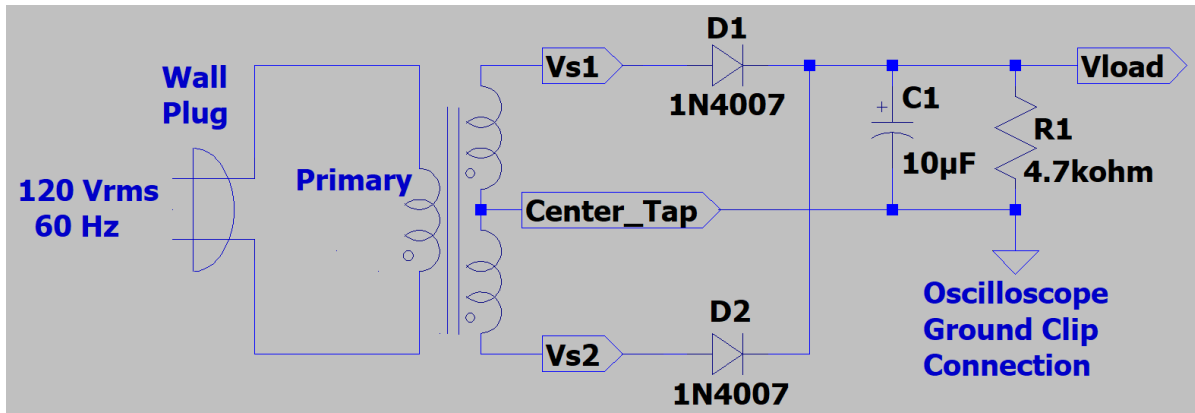


Figure 5: Full-Wave Diode Rectifier Circuit Using a Center-Tapped Transformer.

2. Connect the CH 1 oscilloscope probe to the anode (+) side of either diode D1 or D2, and the CH 2 oscilloscope probe to V_{load} , with both ground clips connected to ground.
Warning: The oscilloscope probe ground clips are connected to earth ground through the oscilloscope AC power cord, meaning that connecting the alligator ground clip to a circuit node shorts that node to earth ground.
3. Adjust the time per division setting near the upper right-hand corner to 5 mS per division.
4. Since the output of the transformer is somewhat noisy, averaging 64 measurements together results in much cleaner results. This is to be accomplished by clicking on the three horizontal lines located just above the settings gear of the Trigger menu near the upper left-hand corner of the oscilloscope screen.
5. Measurement averaging on the VirtualBench oscilloscope can be invoked by means of a **Display Options** menu located in the upper right-hand corner of the Oscilloscope Screen, illustrated in **Figure 1**. Select **Acquisition** → **64 averaged** to reduce random measurement noise.
6. Make sure that the **Mean, RMS, Peak-to-peak** and **High** VirtualBench measurement functions for both CH 1 and CH 2 measurements are still enabled.
7. After double checking your circuit for proper capacitor polarity, etc., turn on the transformer, being ready to turn it off if something is amiss with your connections.
8. If the powered circuit appears to be connected properly, then you should get waveforms that look like the screen capture illustrated in **Figure 6** below after allowing time for the 64 averages to complete.
9. Add both waveform cursors to the V_{load} waveform, with **Type** set to **Track**. Adjust the cursors along the V_{load} waveform such that one cursor is located at a waveform peak, while the other cursor is located at a waveform valley, as illustrated in **Figure 6** below.
10. After the measured values are properly settled and displayed, perform a screen capture of the resulting waveforms and measured values. **Then replace the screen capture in Figure 6 below with your version, leaving in the figure number and caption.** (12 Points.)

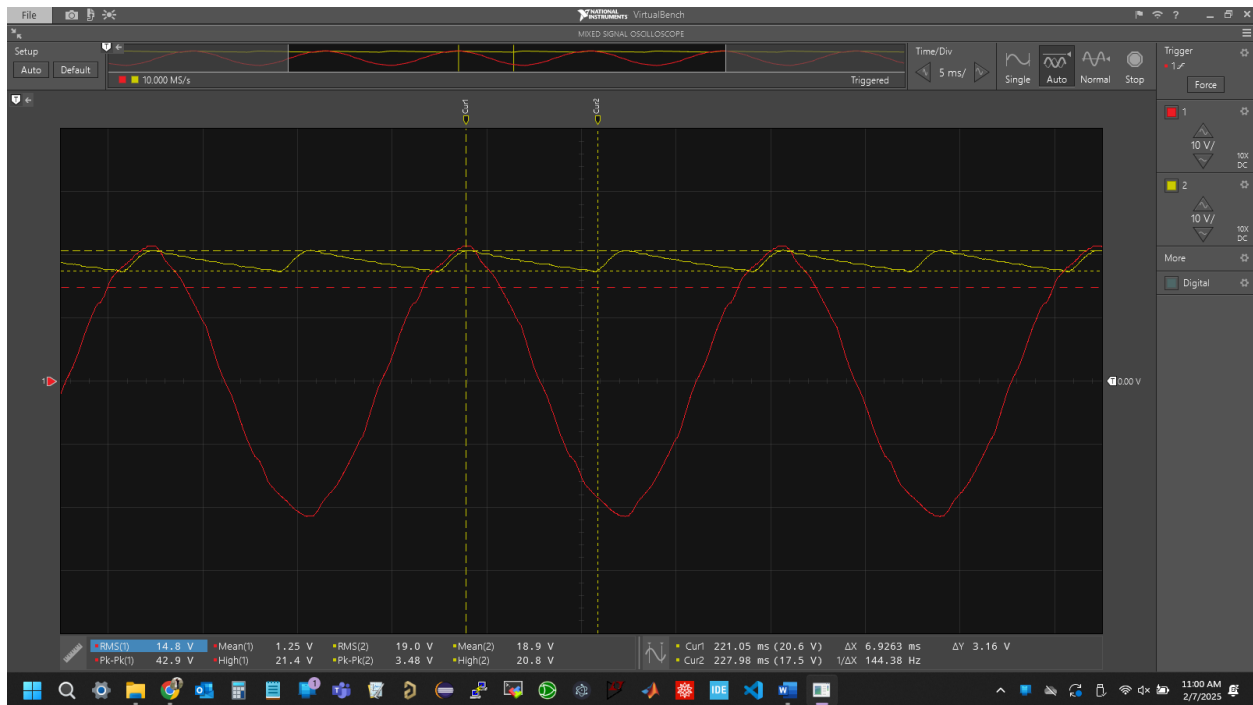


Figure 6: Input and Output Waveforms for the Full-Wave Rectifier Circuit.

11. From your VirtualBench measured results, record below in **Table 2** the **Mean** value of the V_{load} as $V_{load_meas_avg}$, **RMS** value of V_{load} as $V_{load_meas_rms}$ and **cursor ΔY** value of the V_{load} waveform as V_{R_meas} for measured ripple voltage. Be sure to include units for your **Table 2** values. (6 points.)

Table 2: Measured and Simulated Full-Wave Rectifier Values

$V_{load_meas_avg}$	$V_{load_meas_rms}$	V_{R_meas}	$V_{load_sim_avg}$	$V_{load_sim_rms}$	V_{R_sim}
19.0 V	19.0 V	3.24 V	19.31 V	19.33V	2.76 V

Part 3 – LTspice Full-Wave Rectifier

1. Connect up the Full-Wave Rectifier utilizing a center-tapped transformer as shown below in **Figure 8**. The center-tapped transformer is to be included by placing three separate inductors, with inductance values given in **Figure 8**. On the **Edit** pull-down menu in the upper left-hand corner of the LTspice window, choose **.op** Spice Directive, which opens an edit pane in which to add the following inductor coupling information: **K L1 L2 L3 1**, which couples together inductors L1, L2 and L3, forming a transformer. Make sure your polarity dots on the coupled inductors are as shown in the figure for proper phasing. A step-down ratio of 8 is used in this lab to step-down from the 170 V peak to approximately 21 V peak. The step-down ratio in an LTspice transformer constructed from coupled inductors is controlled by the inductance ratios between the primary and secondary.
2. For the 1N4007, first place a standard **diode** from the main LTspice library. Then change the diode type from the generic LTspice silicon pn junction diode to a 1N4007

diode by hovering the hand symbol over the diode and right clicking to open the diode parameter pane, which includes a **Pick New Diode** button. The **Pick New Diode** button opens a **Select Diode** pane with many available diode models, including the 1N4007. Sorting the list by clicking on **Part No.** will position the 1N4007 diode model either near the top or bottom of the list. Click on the 1N4007 Part No. and then click OK to configure the diode symbol on the schematic to use the 1N4007 diode simulation model. The diode type can also be changed simply by editing the value from D to 1N4007 on the schematic.

3. For practical rectifier circuits the output voltage ripple needs to be reduced from the rectified waveform illustrated in **Figure 7**, which is accomplished by the addition of filter capacitor, i.e., C_f in **Figure 8** below. Large value polarized electrolytic capacitors are often used for filter capacitors in rectifier circuits. The **polcap** in the main LTspice component library provides a polarized capacitor symbol.
4. In the **Edit** pull-down menu, add your name to your schematic as follows: **Edit** → **Aa Text**.
5. When completed with your schematic, **replace the schematic shown in Figure 8 below with your version, including your name.** (12 points.)

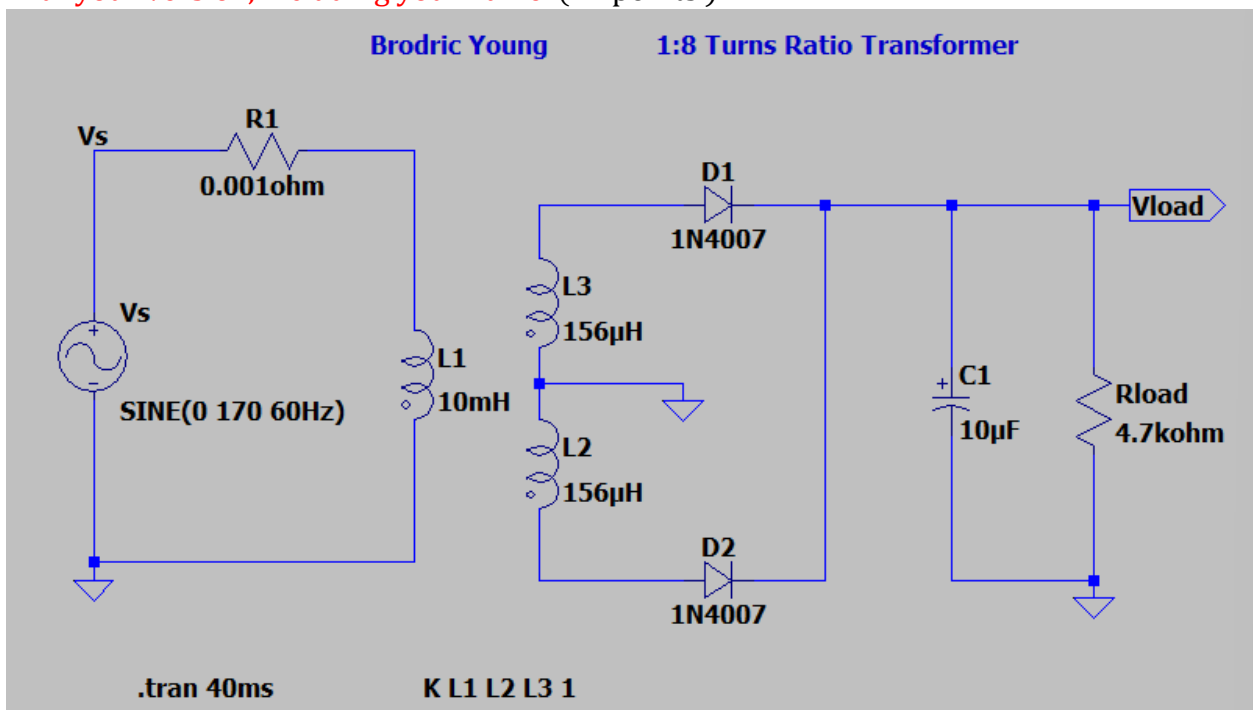


Figure 8. Full-Wave Rectifier Using A Center-Tapped Transformer.

6. After running the transient analysis, add a 2nd plot pane by means of **Plot Settings** → **Add Plot Pane**. Choose to display **V(vload)** in the 1st (top) plot pane and **V(vs)** in the 2nd (bottom) plot pane, as illustrated below in **Figure 9**. With the two plot panes, click on the appropriate pane before invoking the **Plot Settings** → **Add Trace** to get the desired traces associated with the desired plot pane.

7. Attach both cursors to **V(vload)** and then move the cursors to measure the peak-to-peak ripple of the waveform. Then drag the cursor pane onto your plot to document your measured peak-to-peak ripple voltage value as illustrated in the figure below.
8. Annotate your plot pane with your name by means of the **Plot Settings** → **Notes and Annotations** → **Place Text** option available by accessing the **Plot Settings** pulldown menu above the toolbar.
9. By means of **Plot Settings** → **Manual Limits**, or the ruler icon when hovering the cursor near the horizontal axis, set the horizontal axis limits from 10 ms to 40 ms with 5 ms ticks.
10. Hover the mouse over the waveform label at the top of the plot pane, **V(vload)** and when the hand symbol appears, hold down the **Ctrl** key while performing a left mouse click to open a **Waveform** pane indicating Average and RMS values. Move this Waveform pane to a more convenient location on the plot pane. **Replace the resulting screen capture below with your version, including the Waveform Pane indicating the average and RMS values of V(vload).** (9 Points.)

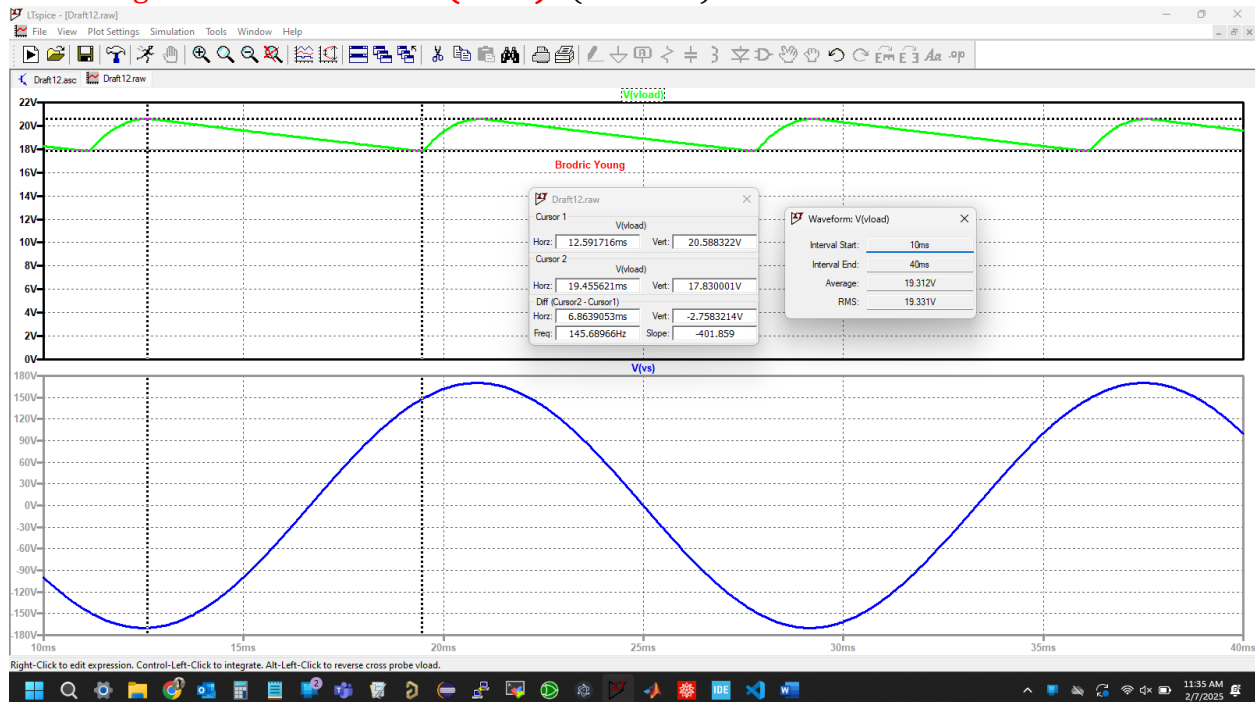


Figure 9. Full-Wave Rectifier Using A Center-Tapped Transformer Simulation Results.

12. Record above in **Table 2** the **Average** value of the V_{load} as $V_{load_sim_avg}$, the **RMS** value of V_{load} as $V_{load_sim_rms}$ and the ΔY cursor value of the V_{load} waveform as V_{R_sim} for measured ripple voltage. Be sure to include units for your **Table 2** values.

Discussion and Conclusions Questions: (For the following questions use your own words along with complete sentences. Points are to be deducted for AI generated answers.)

1. In your own words describe the reason for using a relatively large value capacitor in parallel with the output of the diode rectifier circuits used in this lab. (4 Points.)

Having a capacitor in parallel with the output helps to smooth out the ripple in the rectified voltage. Using a large capacitor is better at smoothing out the ripple because it can hold more charge and therefore supplies current to the load for a longer period of time until the AC signal comes back around and charges it up again.

2. Based on your oscilloscope observations, what was the frequency of the full-wave rectified output signal relative to the frequency of the input signal prior to rectification? (1 Point.)

It looks like about twice as much as the input signal. There's a peak on the output signal at every peak and valley of the input signal which would mean the output is twice the input frequency.

3. The following formula is to be used to estimate the peak-to-peak ripple voltage for given load current and filter capacitor C_f , and ripple frequency of the rectified waveform f_R :

$$V_R = \frac{I_{load}}{f_R C_f}.$$

Calculate the expected peak-to-peak ripple voltage of the full-wave rectifier circuit of **Figure 5**, with I_{load} determined from $V_{load_meas_avg}$ value from **Table 2** and the load resistance of **Figure 5**. (Note that f_R is not equal to the standard US 60 Hz AC Power frequency.) (2 Points.)

$$V_R = \frac{\left(\frac{19V}{4700\Omega}\right)}{(120Hz)(10 * 10^{-6}F)} = 3.37 V$$

Diode Rectifier Lab Grading Rubric: Submit an electronic version of a lab report for credit for this lab. The goal of your lab report is to provide sufficient documentation so that the lab can be repeated if necessary. For your lab report, add a cover page, your results, along with your answers to the Discussion and Conclusions questions to this instruction document. Your cover page is to include class, lab title, author and lab partner. If you worked in a pair, you can share all measured data with your lab partner. However, any simulations along with your Discussion and Conclusions section is to be uniquely yours and not a copy of your lab partners. The rubric below does not need to be included in your lab report.

Lab Report Item	Points
Cover Page	2
Part 1 – Center-Tapped Transformer Reasonable Table 1 Values with Units. (1 point per entry, -0.25 points for each missing unit.)	8
Part 2 – Hardware Full-Wave Rectifier Figure 6: (12 – points total, 1 point for reasonable AC input waveform, 1 point for reasonable rectified DC output waveform, 2 points for proper cursor setup indicating ripple voltage on the output waveform, 8 points for including automatic measurements with 1 point each for automatic measurements of Mean, RMS, Peak-to-peak and High V for each channel.) Table 2: (6 – points total, 1 point per entry, -0.25 points per entry for missing units. Award full credit for dc and rms voltage values ranging from 17 to 20 V, and voltage ripple V_R values ranging from 2.5 to 3.5 V.)	18
Part 3 – LTspice Full-Wave Rectifier Figure 8: (12 points total – 1 point for voltage source with SINE(0 170V 60Hz) configuration statement, 1 point for R1, 1 point for Rload, 1 point for C_f , 2 points for correct inductor connections along with $L1 = 10\text{mH}$ and $L2 = L3 = 156\mu\text{H}$, 2 points for correct diode connections and D1N4007 type and model statement, 1 point for inductor coupling command K L1 L2 L2 1 , 1 point for correct ground connections, 1 point for .tran 40m statement, 1 point for name included on schematic.) Figure 9: (9 points, 1 point for reasonable V(vload) waveform, 1 point for reasonable V(vs) waveform, 1 point for including 2 nd plot pane, 1 point for proper cursor setup indicating ripple voltage on the output waveform, 2 points for including cursor pane on the plot pane, 1 point for Waveform pane included on the plot pane, 1 point for horizontal axis limits of 10 ms to 40 ms, 1 point for including name as annotation.)	21
Discussion and Conclusions	7
Grammar and Professionalism	4
Total	60

Please give feedback on errors you find in this document.